



Assignment

Spring 2026 2nd Semester

Course Title: Circuit Analysis Lab

Course Code: CMPE-121L

Topic(s): Lab 5 Introduction to Proteus

SUBMITTED TO:

Mr. Mehmood-ul-Haq


SUBMITTED BY:

Muhammad Saad (2025-CE-113)


Submission Date: 27 Apr, 2026

Department of Computer Engineering
University of Engineering and Technology Lahore
Main Campus



Experiment 1

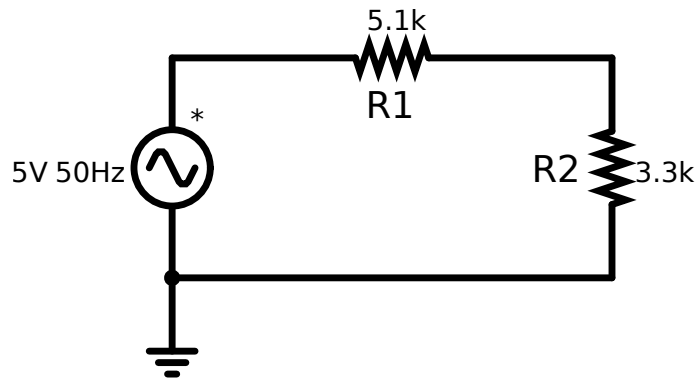

Simulation in Falstad CircuitJS

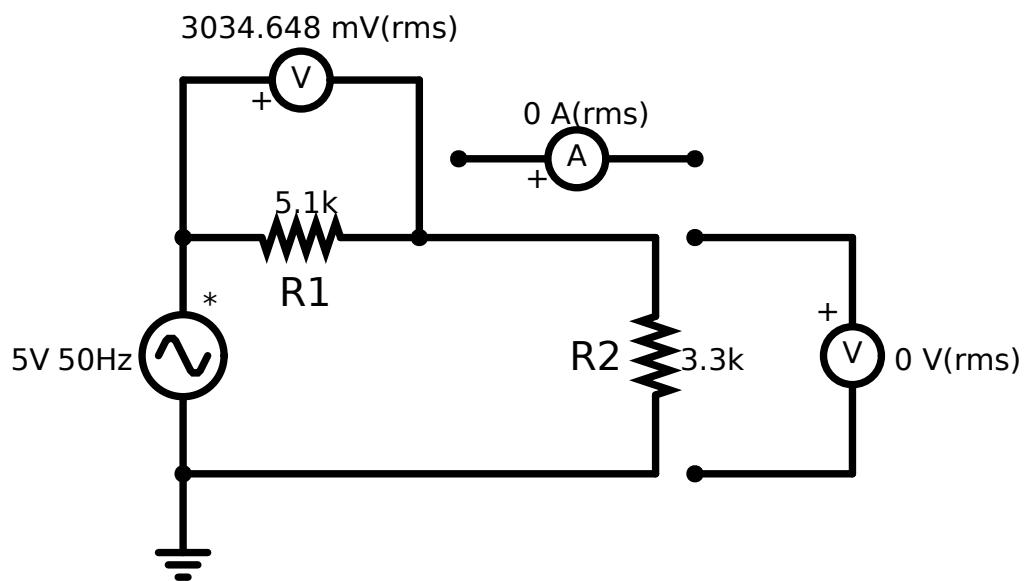

Falstad: Voltage across R_1

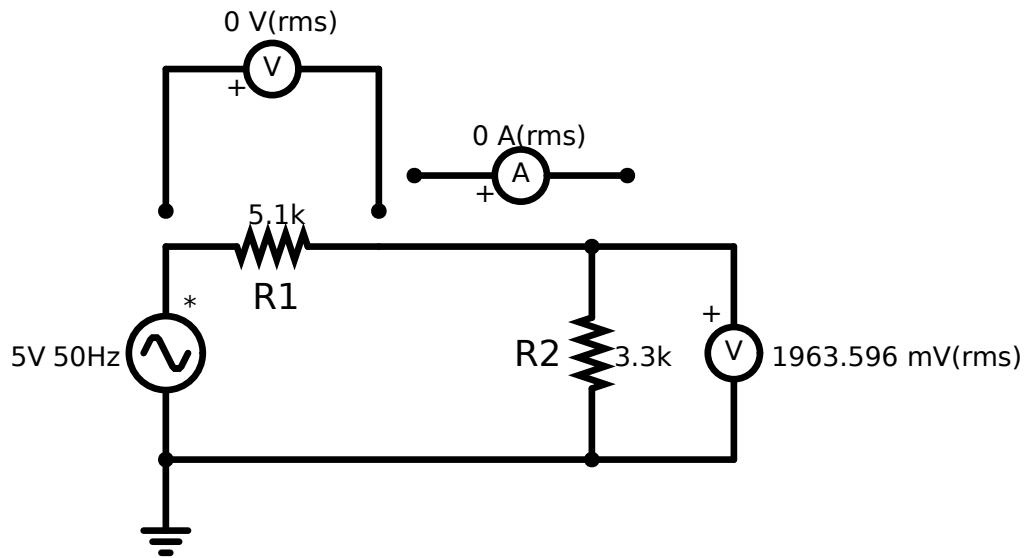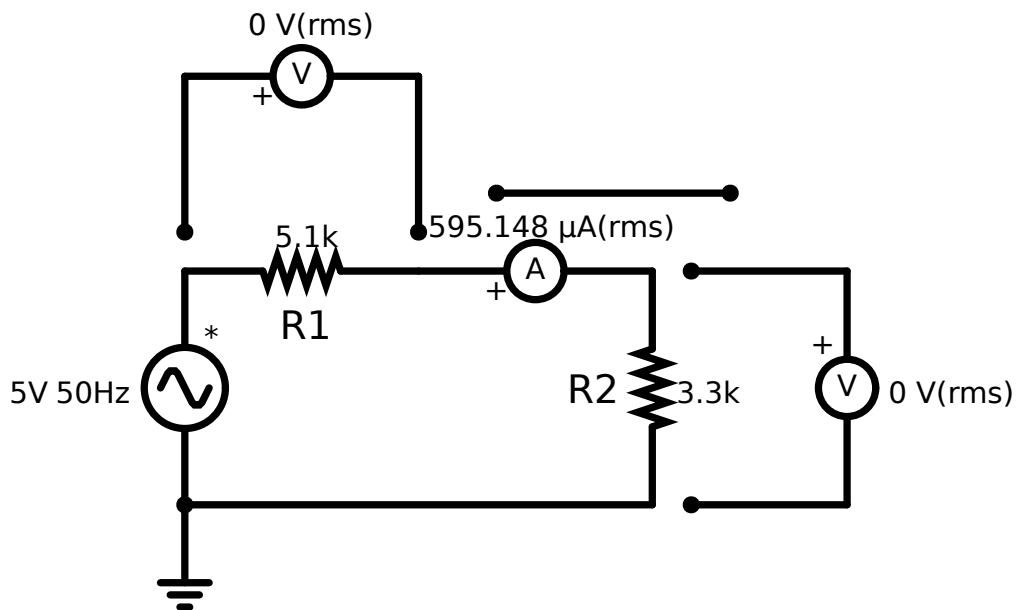
Falstad: Voltage across R_2 Falstad: Current through R_1 and R_2

Experiment 1 Data


Simulated Values

R1 Voltage	R2 Voltage	Current
3.03465 V	1.96360 V	0.59515 mA



Experiment 2

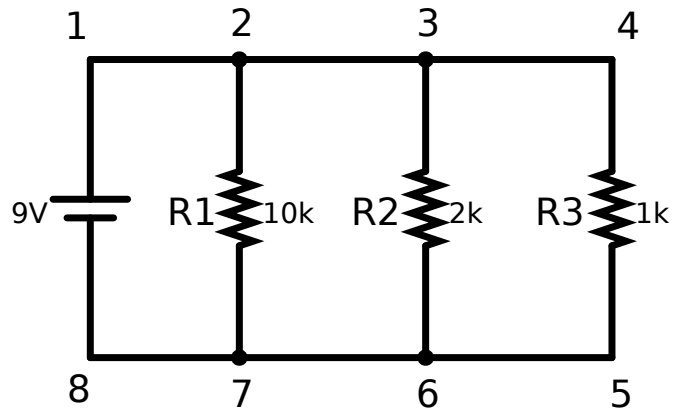


Simulation in Falstad CircuitJS

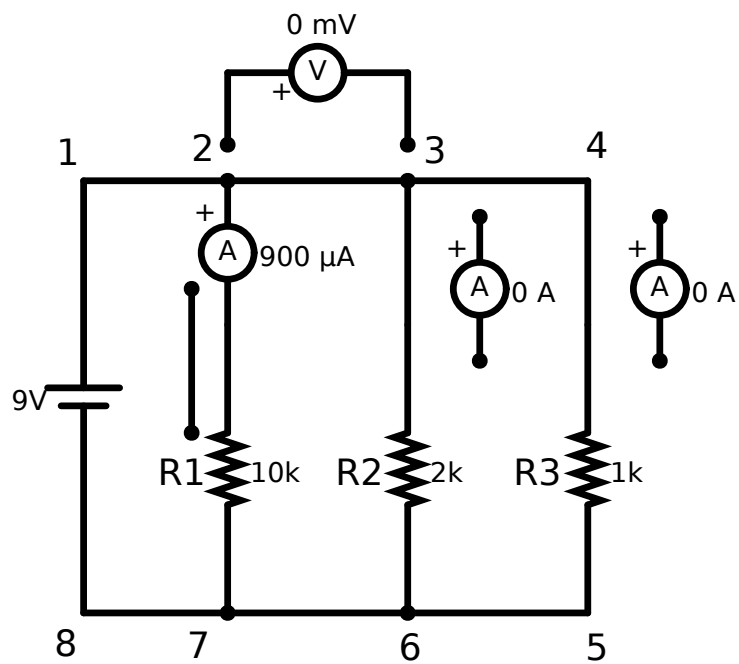

Falstad: Current through R_1

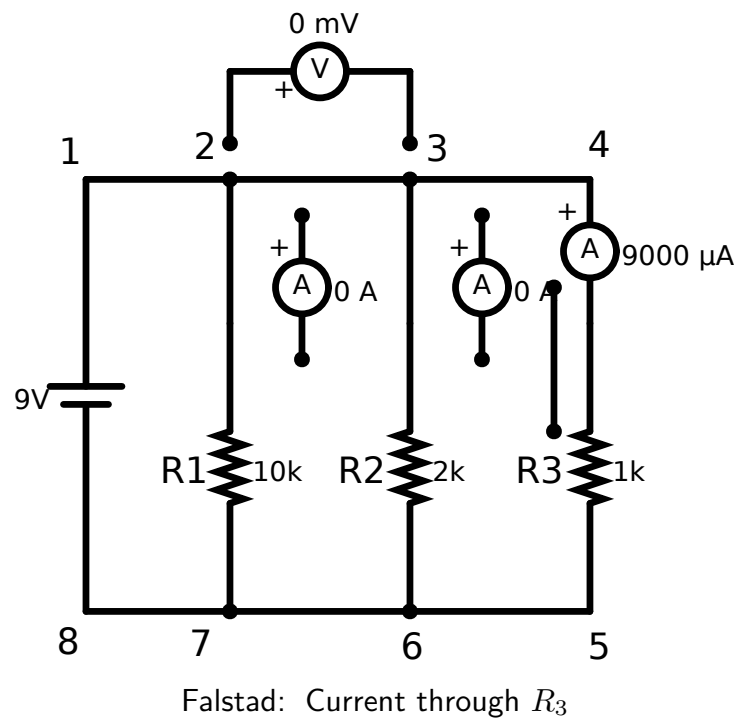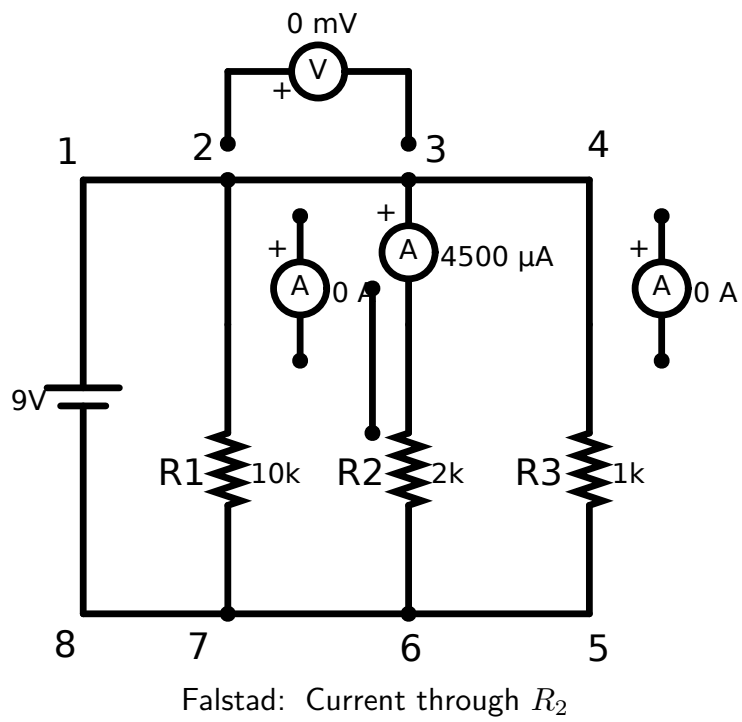

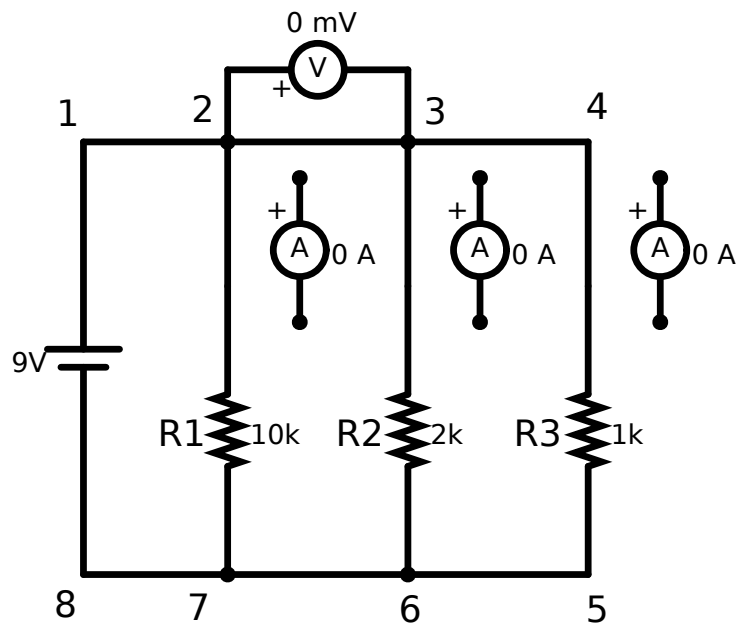

Falstad: Voltage between Node 2 and Node 3

Experiment 2 Data

Simulated Values

R_1 Current	R_2 Current	R_3 Current	Voltage between nodes 2 and 3
0.900 mA	4.500 mA	9.000 mA	0.000 V